

Roll No.

BCA-202(N)

B. C. A. (Second Semester) EXAMINATION, May/June, 2015

(New Course)

Paper Second

DIGITAL ELECTRONICS AND COMPUTER ORGANIZATION

Time: Three Hours]

[Maximum Marks : 75

Note : Section A is compulsory. Attempt any *two* questions from Section B and any *two* questions from Section C.

Section—A

3 each

(Short Answer Type Questions)

1. (A) How many $32\text{ K} \times 1$ RAM chips are needed to provide a memory capacity of 256 K bytes ?
(B) What is the minimum number of gates required to implement the Boolean function $(AB + C)$ if we have to use only 2 input NOR gates ?
(C) Find the minimum number of D flip-flops needed to design a 2^{58} counter.

- (D) Given f_1 , f_2 and f_3 is canonical sum of products form (in decimal) for the circuit.

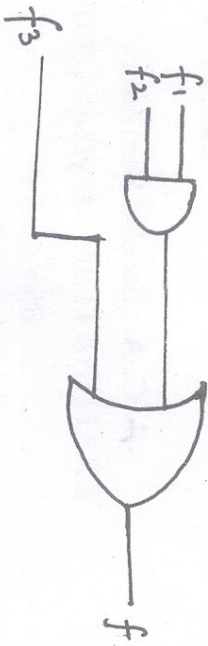


Fig.

$$f_1 = \Sigma m(4, 5, 6, 7, 8)$$

$$f_2 = \Sigma m(1, 6, 15)$$

$$f_3 = \Sigma m(1, 6, 8, 15)$$

then find f_2 .

- (E) Find the output of the following logic diagram.

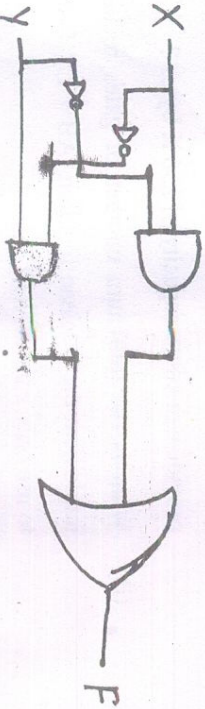


Fig.

- (F) Implement EX-NOR gate with the help of NAND gate. Show the output at each step.
- (G) Express the Boolean function $F = P + Q/R$ in a sum of minterms.
- (H) Simplify the Boolean function :
 $F = (A'BC + AB'C' + ABC + ABC')$
- (I) Explain the JK flip-flop with its working.

Section—B

(Long Answer Type Questions)

2. What is PLA ? A combinational circuit is defined by the functions :

$$F_1(A, B, C) = \Sigma(3, 5, 6, 7)$$

$$F_2(A, B, C) = \Sigma(0, 2, 4, 7)$$

Implement the circuit with PLA having three inputs, four product terms and two outputs.

3. (i) Implement the following function using the don't care conditions :

$$f(c, d, a, b) = \Sigma(0, 2, 6, 8)$$

$$\text{and } d(c, d, a, b) = \Sigma(1, 4, 10)$$

- (ii) What is the use of min terms and max terms ?

4. Design a counter with the following binary sequence : 0, 1, 3, 7, 6, 4 and represent using T flip-flops. 12
5. Write short notes on any *three* of the following : 4 each
- Shaft register
 - Race condition in RS flip-flop
 - Full adder
 - Design procedure of sequential circuits

Section—C

8 each

(Long Answer Type Questions)

6. A RAM chip has a capacity of 1024 words of 8 bits each (1 k × 8). Find the number of 2 × 4 decoders with enable lines needed to construct a 16 k × 16 RAM from 1 k × 8 RAM. 12
7. What is decoder ? Design a BCD to Decimal decoder. 10, 2
8. Draw the block diagram of sequential circuit and discuss it.

Implement the function $F(A, B, C) = \Sigma(1, 3, 5, 6)$ with multiplexer. 2, 10

9. Answer any *three* of the following : 4 each
- Design 4 × 16 decoder with two 3 × 8 decoder
 - Logic diagram of a look ahead carry generator
 - Half-subtractor
 - Simplify the Boolean function :

$$F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$$